


## Suggested Answers to 2016 O level Science Physics 5076/5077/5078 Paper 5

In the 2016 GCE O Level Science (Physics) practical examination, students were asked to measure the resistance of a resistance wire (nichrome wire) using two different formulas.

$$R_1 = \frac{V_L}{I_{\text{standard}}} \quad \text{and} \quad R_2 = \frac{\text{gradient} \times \text{length} (x)}{100 \times I_{\text{standard}}}$$

The length of the resistance wire was 90.5cm (0.905m) and students were asked to derive a  $I_{\text{standard}}$  value between 0.12A and 0.20A on the ammeter. For a current within the 0.12A – 0.20A range, the student had to determine the  $V_L$ , the p.d. across the entire length of the wire, from the voltmeter.

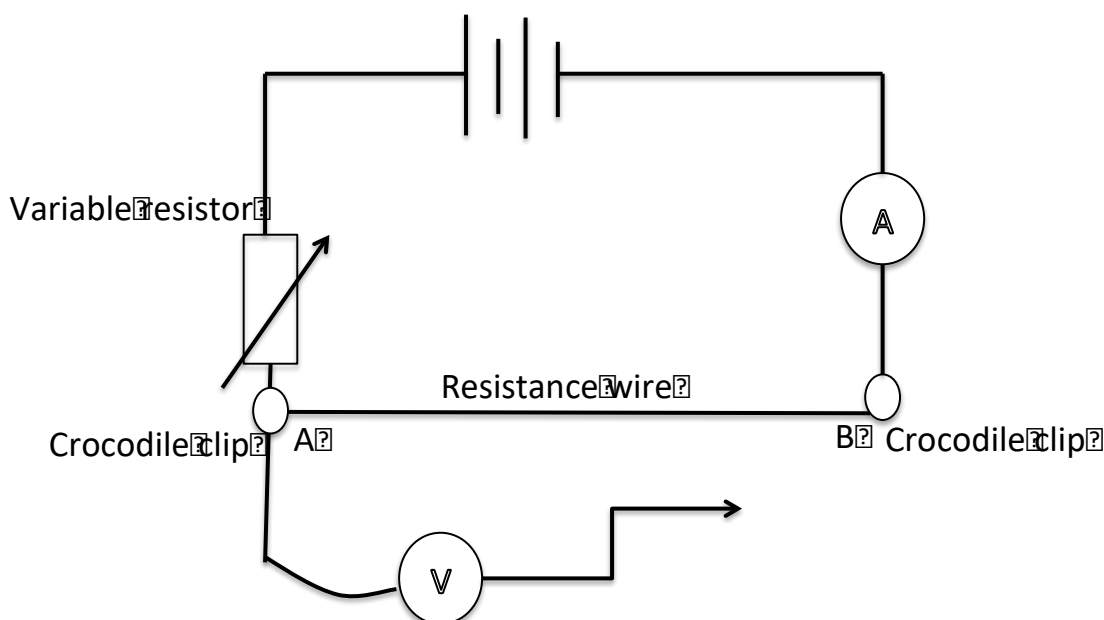Teacher's Comment: Since students were given two 1.5V batteries to be connected in series, the total p.d. must have been 3V. Thus the p.d. across points A and B in the diagram below must also be 3V. As such, if  $V_L = 3V$  and for a range of  $I_{\text{standard}}$  values between 0.12A and 0.20A, students should get  $R_1$  values **between 15Ω and 25Ω**.





Next, to determine  $R_2$ , students were asked to carry out the following:

- i. Measure the length of the wire and record.
- ii. Fix the ammeter from 0.12 to 0.20 A.
- iii. Measure and record  $V_1$  using the 50 cm ruler.
- iv. Measure and record  $V_2$ , which is to pull the clip A to the right so that the wire sticks out of the circuit by 10 to 20 cm.
- v. Find the average  $V$ .
- vi. Repeat the experiment using lengths between 0 cm to 50 cm.
- vii. Plot Average Voltage against Length and find the gradient of the graph.

Length $x/cm$	Voltage $V_1/V$	Voltage $V_2/V$	Average Voltage $V_{ave}/V$
10			

**Teacher's Comment:** Since  $R_1$  must be equal to  $R_2$ , working backwards, the gradient of the straight line must be **3.31**, for a nichrome wire with resistivity  $1.5 \times 10^{-6}$ .

**Question:** A student wound up the nichrome wire around clip A to make it secure. How will this affect the reading of the resistance  $R_2$ ?

**Teacher's Comment:** As the crocodile clip is a good electrical conductor, when the wire is coiled around the clip, the wire will be in contact with the conductor hence causing the current to flow through a greater length. Since  $R = \frac{\rho l}{A}$ , the resistance of the wire will increase therefore  $R_2$  value will be greater.